

Problem 3.26 Apply mesh analysis to find the mesh currents in the circuit of Fig. P3.26. Use the information to determine the voltage V .

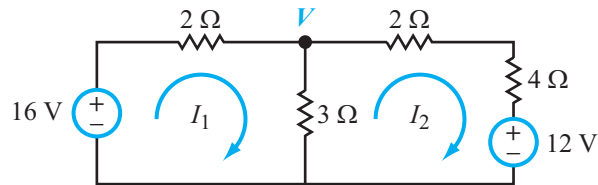


Figure P3.26: Circuit for Problem 3.26.

Solution: Application of KVL to the two loops gives:

$$\text{Mesh 1:} \quad -16 + 2I_1 + 3(I_1 - I_2) = 0,$$

$$\text{Mesh 2:} \quad 3(I_2 - I_1) + (2 + 4)I_2 + 12 = 0,$$

which can be simplified to

$$5I_1 - 3I_2 = 16 \quad (1)$$

$$-3I_1 + 9I_2 = -12. \quad (2)$$

Simultaneous solution of (1) and (2) leads to

$$I_1 = 3 \text{ A}, \quad I_2 = -\frac{1}{3} \text{ A}.$$

Hence,

$$V = 3(I_1 - I_2) = 3\left(3 + \frac{1}{3}\right) = 10 \text{ V}.$$